

Find the sending impedance of the line having negligible losses, where Z_0 is 55Ω , receiving end impedance $155 + j75\Omega$ and line is 1.183 times of wavelength.

$$Z_0 = 55\Omega$$

$$Z_R = 155 + j75\Omega$$

$$l = 1.183\lambda$$

$$\lambda = \frac{2\pi}{\beta}$$

$$\beta = \frac{2\pi}{\lambda}$$

$$l = 1.183\lambda$$

$$\beta l = \frac{2\pi}{\lambda} (1.183)\lambda$$

$$\beta l = 2\pi(1.183) = (2 \times 3.14 \times 1.183)$$

$$\beta l = 7.429 \Rightarrow \boxed{\beta l = 7.43}$$

$$= 55 \left[\frac{(155 + j75) + j(55) \tan(7.43)}{55 + j(155 + j75) \tan(7.43)} \right]$$

$$= 55 \left[\frac{(155 + j75) + j(55)(2.29)}{55 + (155j - 75)(2.29)} \right]$$

$$= 55 \left[\frac{155 + j75 + 122.045j}{55 + 343.94j - 166.425} \right]$$

$$= 55 \left[\frac{155 + 197.045j}{-11.425 + 343.94j} \right]$$

$$= 55 \left[\frac{250 - 702 \angle 51.811}{361.54 \angle 107.950} \right]$$

$$= 55 \cdot [0.693 \angle -56.139]$$

$$Z_{in} = 38.115 \angle -56.139 \text{ (}\Omega\text{)}$$

$$Z_{in} = 21.237 - 31.650j$$

2] A transmission line of characteristic impedance 600Ω is terminated by a reactance of $j150\Omega$. Find input impedance of a section 25cm long at a frequency of 300 MHz .

Sol:

Given, $Z_0 = 600\Omega$

$$f = 300\text{ MHz}$$

$$l = 25\text{cm} \Rightarrow l = 25 \times 10^{-2}\text{m}$$

$$Z_T = j150$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{300 \times 10^6}$$

$$= \frac{300 \times 10^6}{300 \times 10^6}$$

$$\boxed{\lambda = 1}$$

$$\beta = \frac{2\pi}{\lambda} = 6.28$$

$$\beta l = 6.28 \times 25 \times 10^{-2}$$

$$= 1.57 \times 57.3$$

$$\beta l = 89.961$$

$$Z_{in} = Z_0 \left[\frac{Z_R + jZ_0 \tan(\beta l)}{Z_0 + jZ_R \tan(\beta l)} \right]$$

$$= 600 \left[\frac{j150 + j600 \times 89.961}{600 + (-150) \times 89.961} \right]$$

$$= 600 \left[\frac{54126.6j}{-40924.15} \right]$$

$$= 600 [-32403j]$$

$$Z_{in} = 2304.2 \Omega$$

3] A transmission line with a Z_0 of 300Ω is terminated in a purely resistive load. It is found by measurement and the maximum value is $7.5 \mu V$. Calculate the value of load resistance.

Given, $Z_0 = 300 \Omega$

$$V_{max} = 7.5 \mu V$$

$$V_{min} = 5 \mu V$$

Sol.

The standing wave ratio is

$$S = \left| \frac{V_{max}}{V_{min}} \right| = \frac{7.5 \times 10^{-6}}{5 \times 10^{-6}}$$

$$S = 1.5$$

SWR with relation of 'k' is,

$$k = \frac{S-1}{S+1} = \frac{1.5-1}{1.5+1}$$

$$= \frac{0.5}{2.5}$$

$$\boxed{k = 0.33}$$

W.K.T,

$$k = \frac{Z_P - Z_0}{Z_P + Z_0}$$

$$0.33 = \frac{Z_P - 300}{Z_P + 300}$$

$$Z_P - 300 = 0.33Z_P + 99$$

$$Z_P - 0.33Z_P = 399$$

$$Z_P (1 - 0.33) = 399$$

$$\boxed{Z_P = 595.522 \Omega}$$

4] Determine the following i] standing wave ratio
ii] load admittance iii] Impedance of transmission line
at the maximum and minimum of the stationary
waves along the line. The Distance between the
load and the first voltage maximum for the
transmission line with characteristic impedance of
 50Ω with a receiving end impedance of $100 + 12j \Omega$ the

wavelength of the electrical signal along the line is 2.5m .

Given. $Z_0 = 50 \Omega$

$$Z_R = 100 + 121j$$

$$\lambda = 2.5\text{m}$$

Soln:

To find Normalized load impedance.

$$Z_n = \frac{Z_R}{Z_0} = \frac{100 + 121j}{50} = \frac{156.91 \angle 50.43}{50}$$
$$= 3.14 \angle 50.43$$

$$Z_n = 2.0 + 2.4j$$

i) $S = 5.2$

ii) Load Admittance

$$Y_n = \frac{1}{Z_n} = \frac{1}{2 + 2.4j} = \frac{1}{3.12 \angle 50.19} = 0.32 \angle -50.19$$

$$Y_n = 0.2 - 0.25j$$

$$Y_R = \frac{Y_n}{Z_0} = \frac{0.2 - 0.26j}{50} = \frac{0.33 \angle -52.43}{50}$$

$$= 6.6 \times 10^{-3} \angle -52.43$$

$$= 4.02 \times 10^{-3} - 5.2 \times 10^{-3}j$$


$$= 0.004 - j0.0052$$

iii) $I_{\max} = \text{SWR} = 5.2 \Rightarrow I_{\max} = Z_0 I_{\max}(\text{in}) Z_0(s)$
 $= 50(5.2) = 260 \Omega$

$$I_{\min} = \frac{1}{\text{SWR}} = \frac{1}{5.2} = 0.19$$

$$I_{\min} = I_0 I_{\min} \text{ (or) } \frac{I_0}{S}$$

$$I_{\min} = 50 (0.19) = 9.5 \text{ A}$$

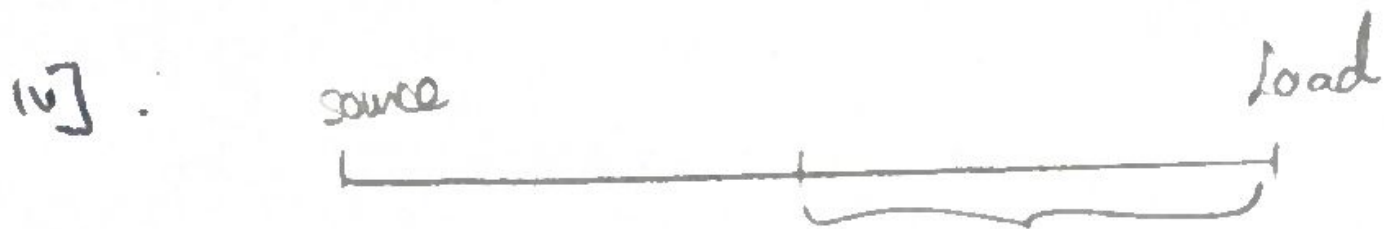

$\rightarrow$ half of full circle $\rightarrow$ because full circle is 0.5. They ask only 1st half
 $= 0.25\lambda - 0.21\lambda$ max so, $\frac{0.5}{2} = 0.25$



$$= 0.039\lambda \quad \therefore \lambda = 2.5 \text{ m}$$

$$= 0.039 (2.5)$$


$$= 0.095$$

1

52

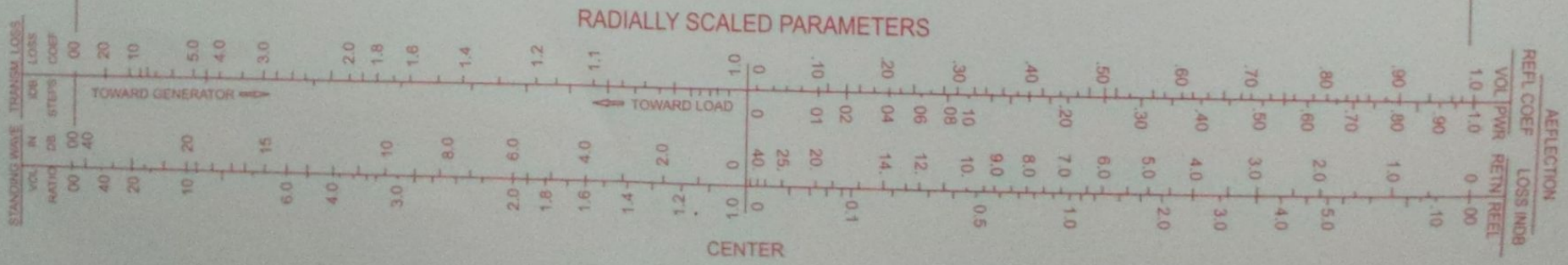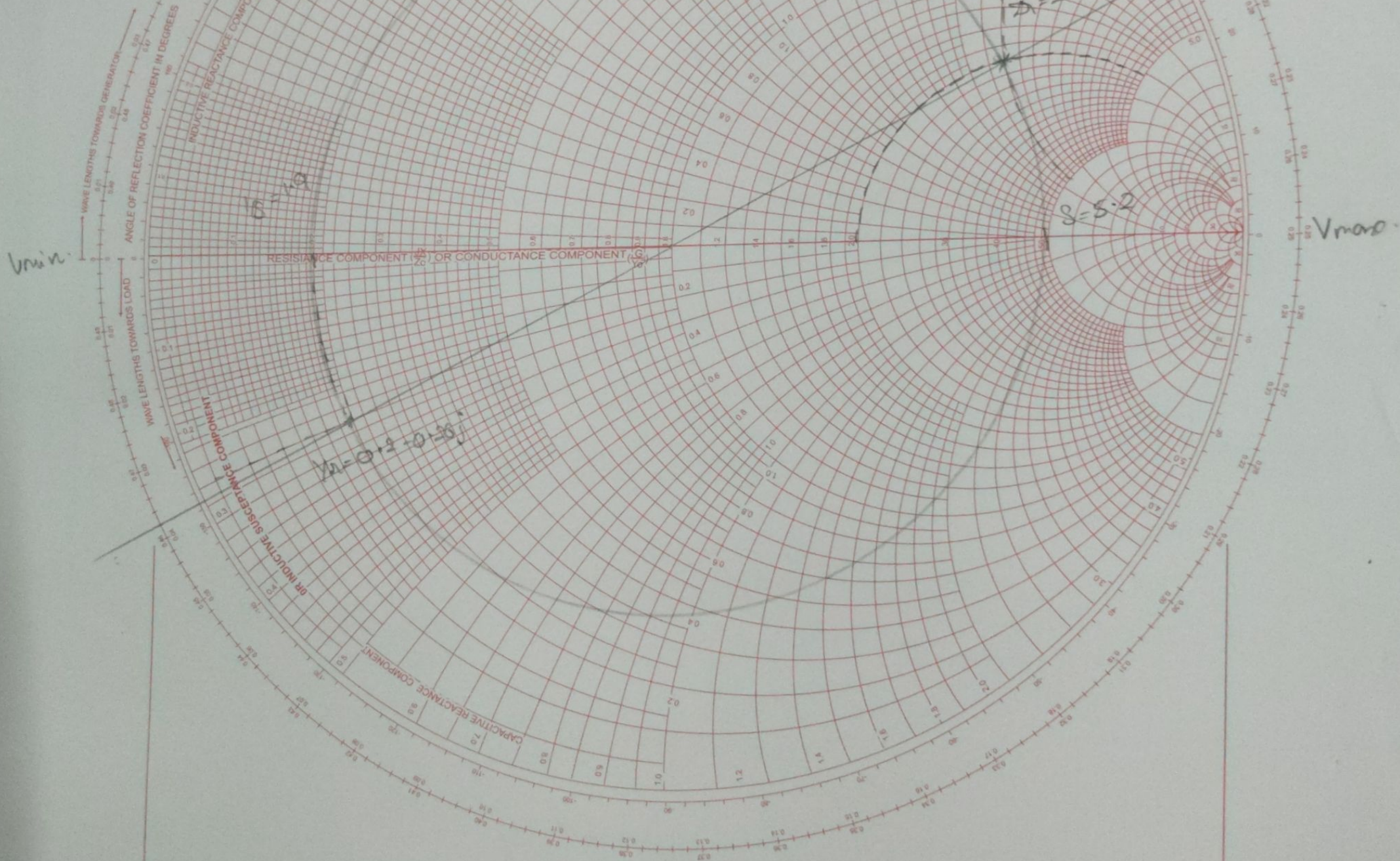

SMITH CHART

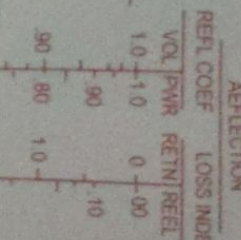

5] Determine the input impedance and standing wave ratio for a distance 1.25λ long transmission line at the sending end with a characteristic impedance 50Ω and load impedance $Z_R = 30 + 40j\Omega$.

Given, $Z_0 = 50\Omega$

$$Z_R = 30 + 40j$$

Sol.

Normalized load impedance,

$$Z_n = \frac{Z_R}{Z_0} = \frac{30 + 40j}{50}$$

$$= \frac{50 \angle 53.13}{50}$$

$$= 1 \angle 53.13$$

$$Z_n = 0.6 + 0.8j$$

$$i] SWR = 2.89, \quad ii] Z_{in} = 0.6 - 0.8j, \quad Z_{in} = 30 - 40j$$

③ Soln.

$$= 0.125 \lambda + 1.35 \lambda$$

$$= 1.375$$

$$= 140.375$$

$$0.105 \lambda$$


$$Z_L = 0.6 + 0.2j$$

$$S = 2.89$$

$$0.375$$

SC
 $I_p = 0$
 I_{in}

OC
 $I_p = \infty$
 I_{in}

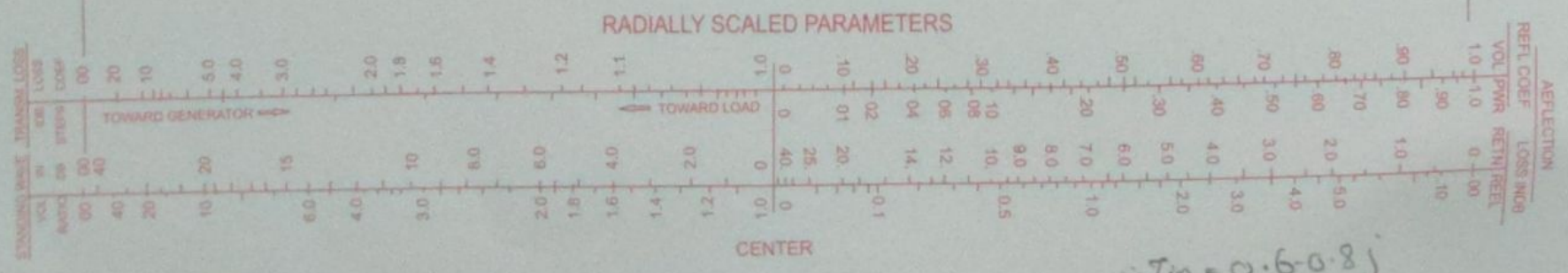

SMITH CHART

$$Z_{in} = 0.6 - 0.8j$$

$$Z_{in} = Z_0 \Gamma_L = (0.5 - 0.8j)(50)$$

$$= 30 - 40j$$

6 A 75Ω lossless transmission line is to be matched with a $100 - j80 \Omega$ load using single stub. Calculate stub length and its distance from the load correspond to the frequency of 30 MHz using Smith chart.

Sol:

$$Z_0 = 75 \Omega$$

$$Z_L = 100 - j80 \Omega$$

$$f = 30 \text{ MHz} = 30 \times 10^6$$

$$Z_L = Z_0 Z_L$$

$$Z_L = \frac{Z_L}{Z_0}$$

$$= \frac{100 - j80}{75}$$

Normalized load impedance,

$$Z_L = 1.33 - j1.06j$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{30 \times 10^6}$$

$$= 10 \times 10^2 = 10 \text{ m}$$

$$= 1000 \text{ cm}$$

$$Y_L = \frac{1}{1.33 - j1.067j} = 0.457 + j0.365$$

$\frac{1}{Z_L}$

$$b = 0.096\lambda$$

$$= 0.096 \times 10$$

$$b = 0.96 \text{ m}$$

$$\lambda t = 0.128 \lambda$$

$$= 0.128 \times 10$$

$$\lambda t = 1.28 \text{ m}$$

distance (l) = 0.096λ

0.162λ


0.066λ

0.318λ

Stub length (l) = 0.128λ

load
imp (Z)
ad (Y)

RADIALLY SCALED PARAMETERS

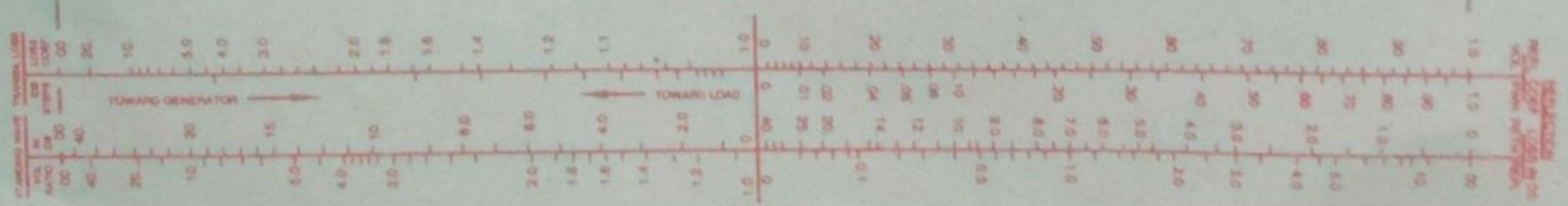

CENTER

SMITH CHART

7. For a transmission line with $Z_0 = 75 \Omega$ and a load with the capacitive impedance $Z_L = 45 - j100 \Omega$. Determine SWR, stub length, stub location by using Smith chart.

Soln: $Z_0 = 75 \Omega$

$$Z_L = 45 - j100 \Omega$$

$$Z_L = Z_0 \Gamma_L$$

$$\Gamma_L = \frac{Z_L}{Z_0}$$
$$= \frac{45 - j100}{75}$$

$$\boxed{\Gamma_L = 0.6 - j1.333j}$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{0.6 - j1.33j} = 0.281 + j0.624j$$

Stub location:

$$b = 0.182\lambda - 0.093\lambda$$

$$\boxed{b = 0.089\lambda}$$

Stub length:

$$l = 0.331\lambda - 0.25\lambda$$

$$\boxed{l = 0.081\lambda}$$

8. For a transmission line with $Z_0 = 300 \Omega$ & a load with a complex impedance $Z_L = 390 + j600 \Omega$. Determine SWR, stub location, stub length for a single stub matching using smith chart.

Soln:

$$Z_0 = 300 \Omega$$

$$Z_L = 390 + j600 \Omega$$

$$Z_L = Z_0 \Gamma_L$$

$$\Gamma_L = \frac{Z_L}{Z_0} = \frac{390 + j600}{300} = 1.3 + 2j$$

$$\begin{aligned} \Gamma_L &= \frac{1}{\Gamma_L} = \frac{1}{1.3 + 2j} \\ &= 0.228 - 0.351j \end{aligned}$$

Stub location:

$$D = 0.261\lambda$$

Stub length:

$$L = 0.081\lambda$$

